



Faculty of Engineering and Technology

JAMIA MILLIA ISLAMIA

TEAM

MAYANK DUTTA


HAIDER ALI

KASHIF ZUHAIR


RECIPROCAL PROPERTY

?

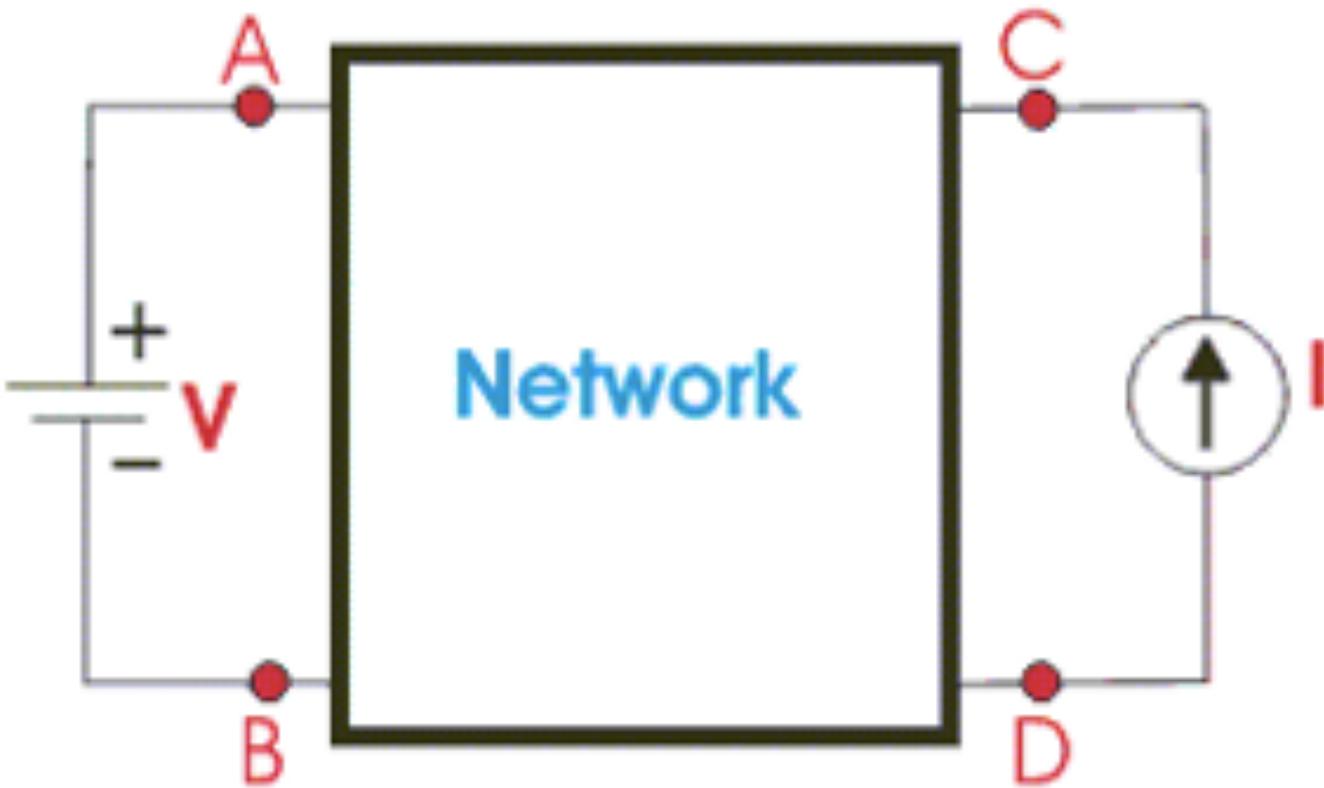
■ In electrical network you might have seen that after inter-changing the Ammeter with the voltage source the reading remains the SAME !!



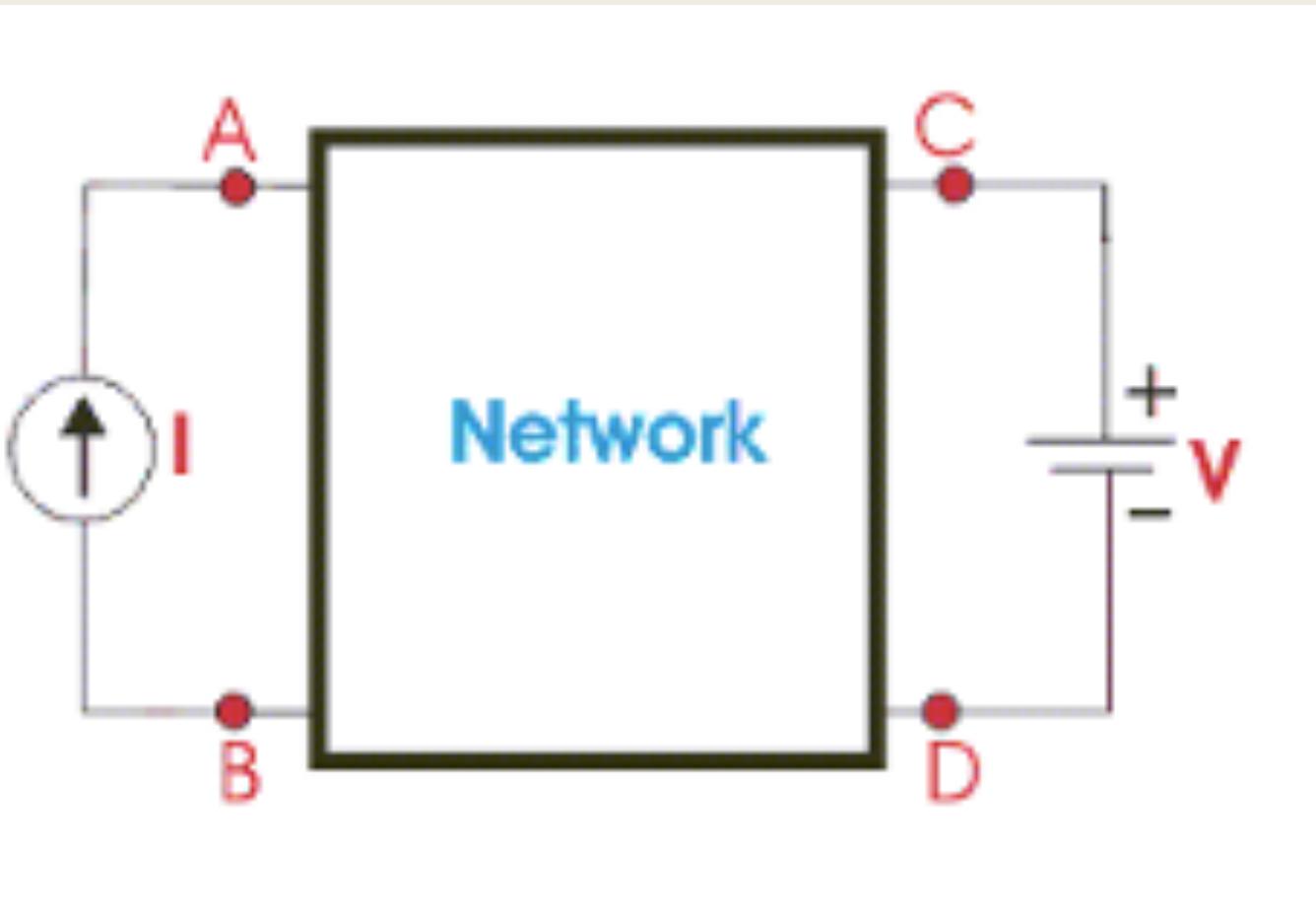- In electrical network you might have seen that after inter-changing the Ammeter with the voltage source the reading remains the SAME !!



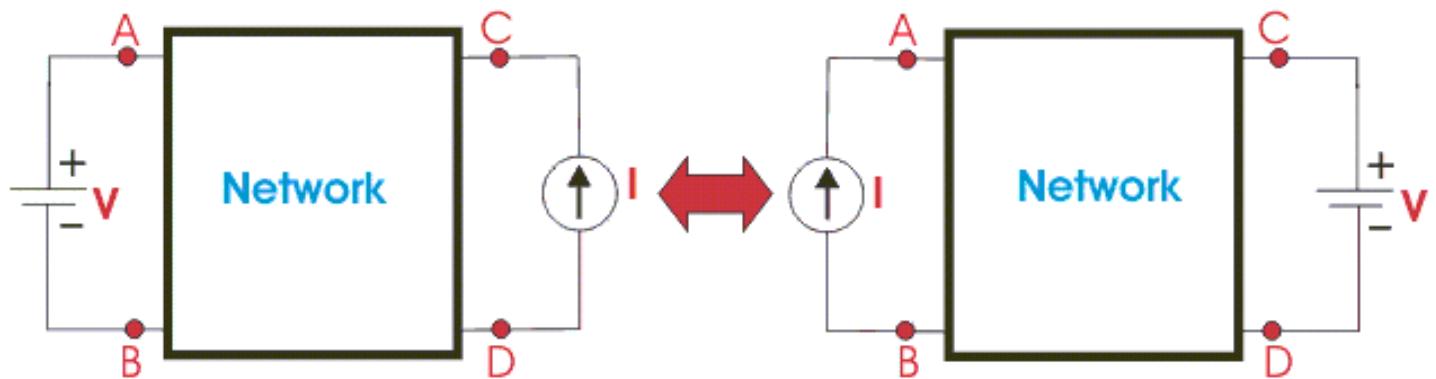- In electrical network you might have seen that after interchanging the Ammeter with the voltage source the reading remains the SAME !!



- In electrical network you might have seen that after inter-changing the Ammeter with the voltage source the reading remains the SAME !!
- This is where the property this property of RECIPROCAL came into the picture,
And the circuit following this property is said to be the reciprocal circuit.

RECIPROCITY THEOREM

By Mayank Dutta

STATEMENT

In a BIDIRECTIONAL SINGLE SOURCE network
the ratio of response to excitation remains the
same even when the positions of the response and
excitation are interchanged.



LINEAR, BIDIRECTIONAL NETWORK
WITH ONE INDEPENDENT SOURCE



V_X : VOLTAGE SOURCE

I_Y : CURRENT DUE TO V_X

Exc.



V_x



N


Res.




I_y

V_x IS OUR EXCITATION
 I_y IS OUR RESPONSE

ON INTERCHANGING THE POSITIONS

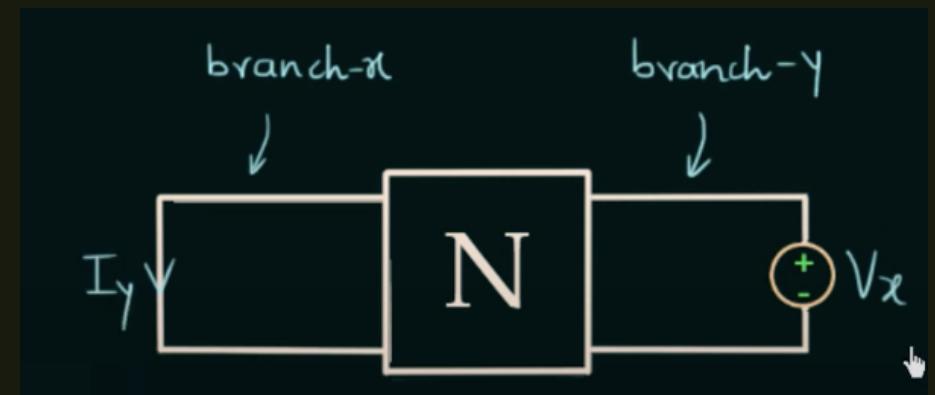

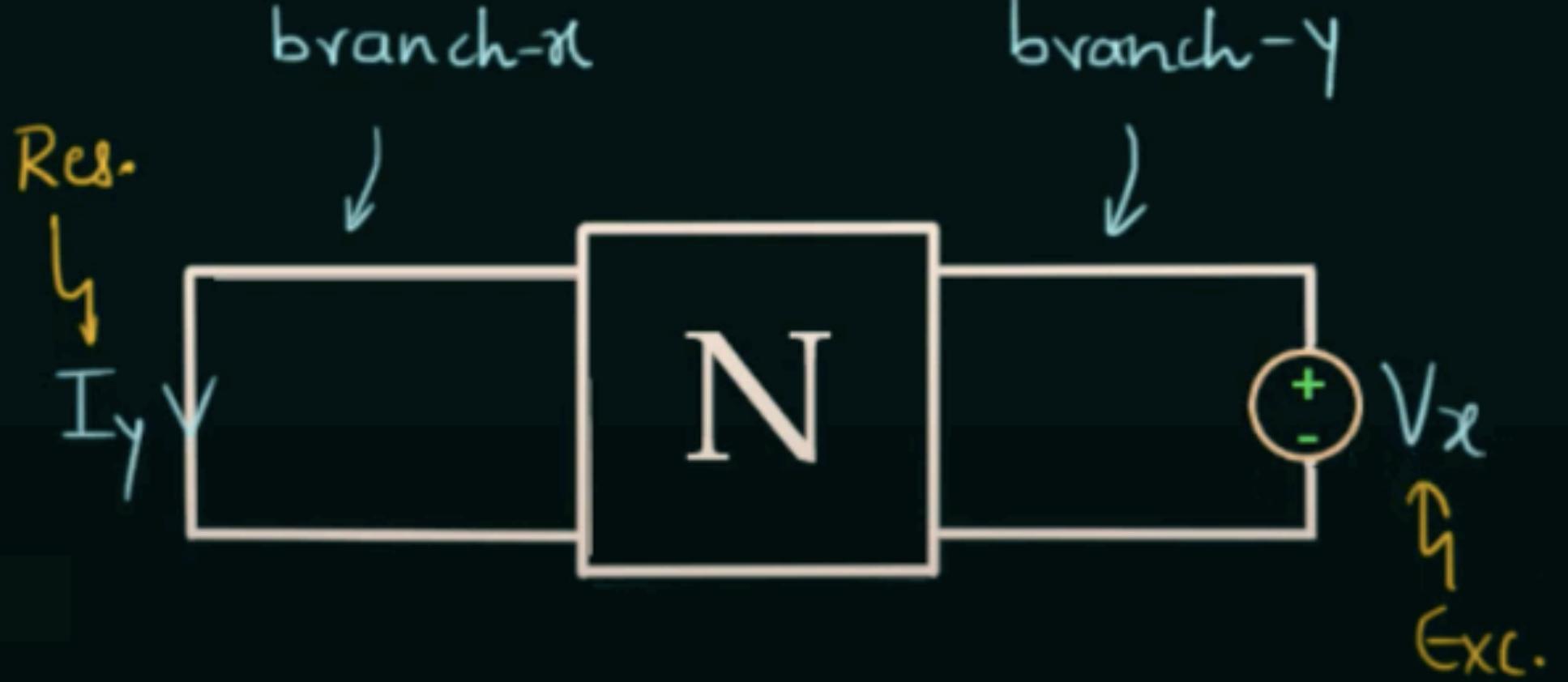

OUR EXCITATION AND RESPONSE WILL ALSO CHANGE BUT THE RATIO WILL BE THE SAME.



E X A M P L E







FIND THE VALUE OF I WHEN THE NETWORK SATISFIES THE RECIPROCITY CONDITIONS.




LET'S
ANALYZE

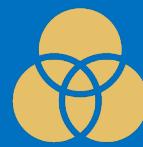


Is there independent
source ?

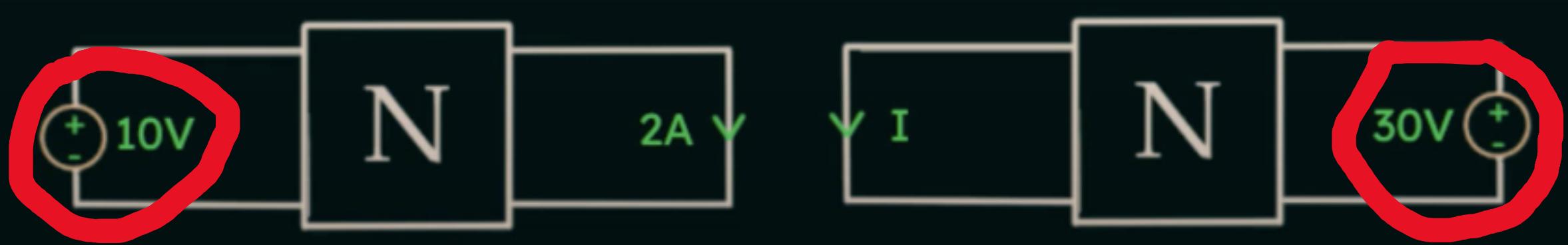


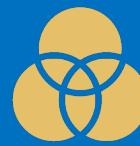


Is there independent
source ?

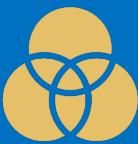

Is there independent source ?


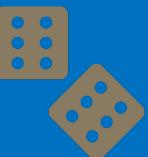


Is there any
dependent source ?

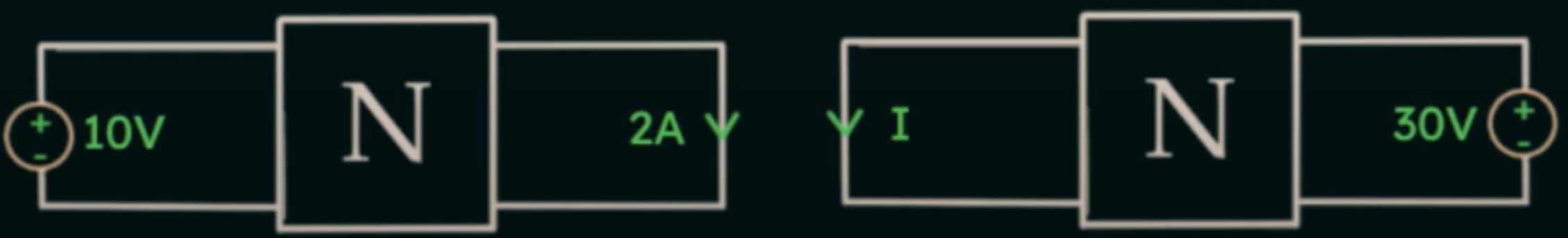





Is there independent source ?

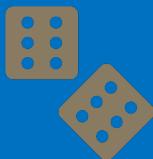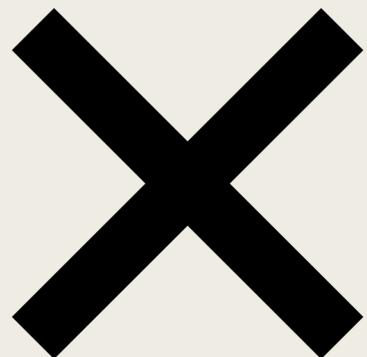

Is there any
dependent source ?

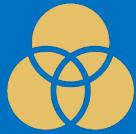

Is there independent source ?

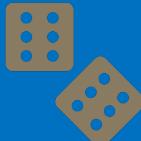

Is there any dependent source ?



Is that circuit
satisfying the
reciprocal properties.




FIND THE VALUE OF I WHEN THE NETWORK
SATISFIES THE RECIPROCITY CONDITIONS.




Is there independent source ?




Is there any dependent source ?

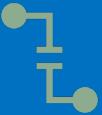

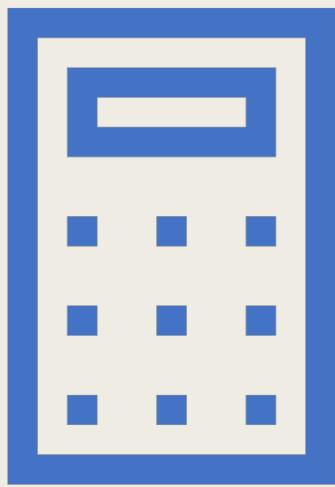
Is that circuit satisfying
the reciprocal
properties?



CALCULATIONS

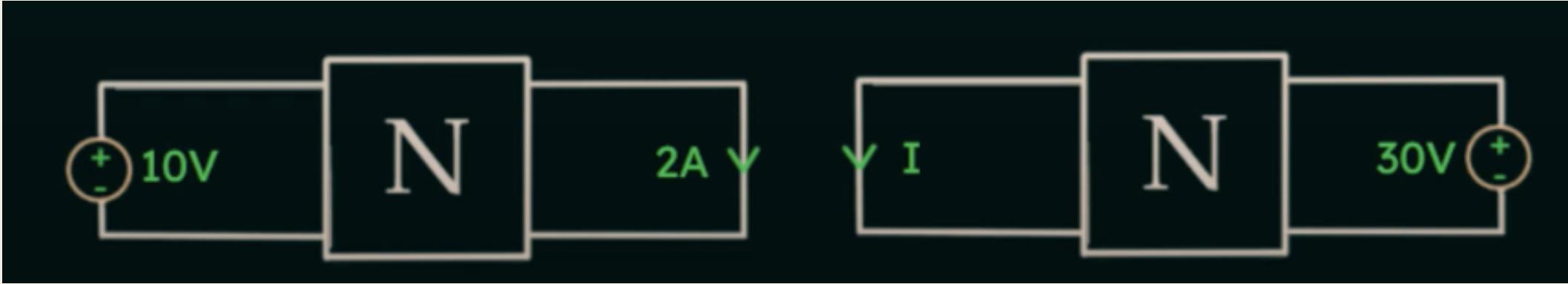

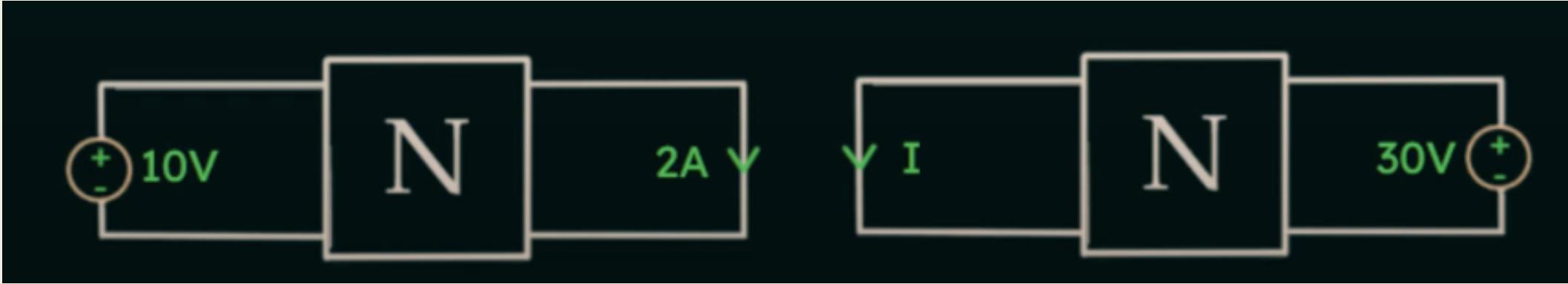
- For right circuit : $(\text{Res} / \text{Exc}) = 2 / 10$




- For right circuit : $(\text{Res} / \text{Exc}) = 2 / 10$
- For left circuit : $(\text{Res} / \text{Exc}) = i / 30$

ACCORDING TO
RECIPROCITY THEOREM




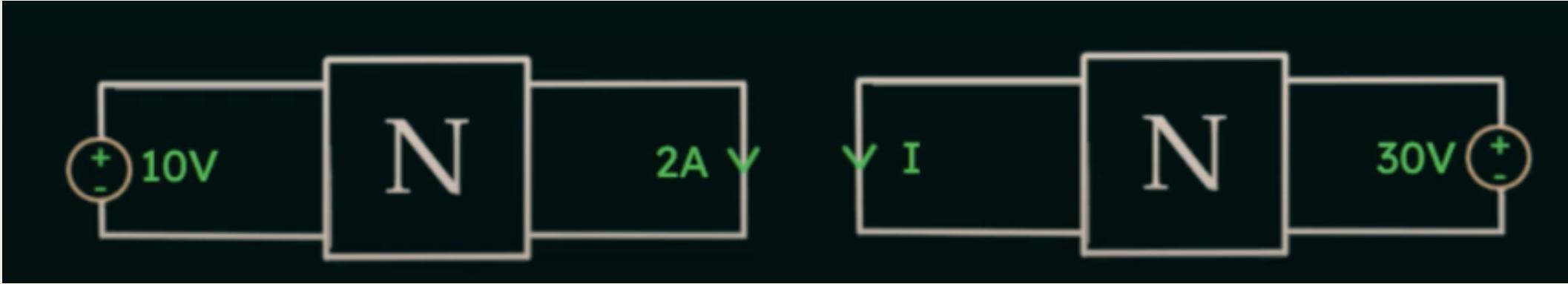

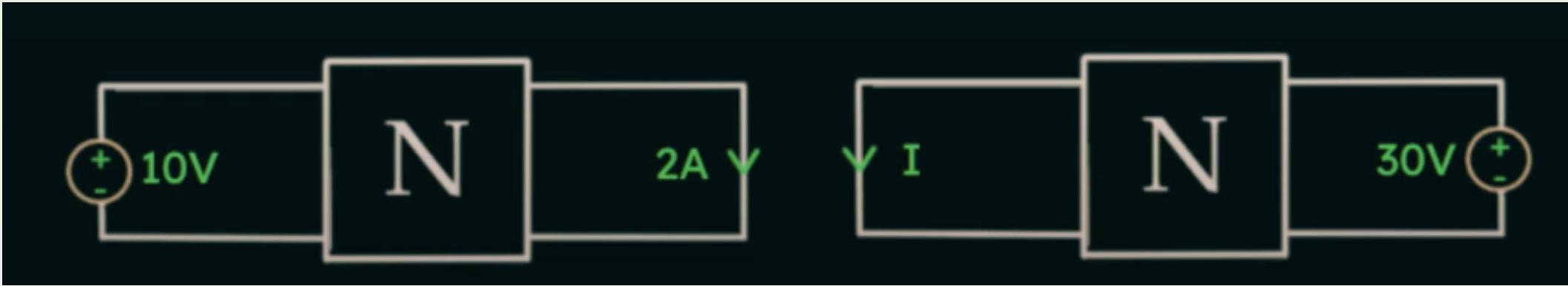- For right circuit : $(\text{Res} / \text{Exc}) = 2 / 10$
- For left circuit : $(\text{Res} / \text{Exc}) = i / 30$
- ACCORDING TO RECIPROCITY THEOREM
- $i / 30 = 2 / 10$



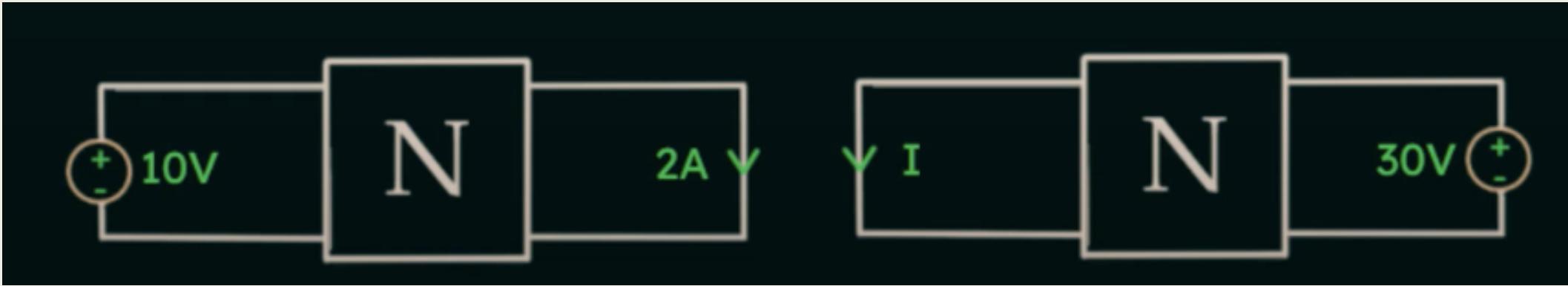- For right circuit : $(\text{Res} / \text{Exc}) = 2 / 10$
- For left circuit : $(\text{Res} / \text{Exc}) = i / 30$
- ACCORDING TO RECIPROCITY THEOREM
- $i / 30 = 2 / 10$
- $i = 6 \text{ Amp.}$



- For right circuit : $(\text{Res} / \text{Exc}) = 2 / 10$
- For left circuit : $(\text{Res} / \text{Exc}) = i / 30$
- ACCORDING TO RECIPROCITY THEOREM
- $i / 30 = 2 / 10$
- $i = 6 \text{ Amp.}$ [Our answer]

HAIDER_ALI

CONDITIONS

Reciprocity theorem will be applicable when.

The ratio of response to excitation is either Ohm or Mho.

Only one independent source is present in the circuit

No dependent source is present in the circuit

Reciprocity theorem will be applicable when.

The ratio of response to excitation is either Ohm or Mho.

Only one independent source is present in the circuit


No dependent source is present in the circuit

Reciprocity theorem will be applicable when.

The ratio of response to excitation is either Ohm or Mho.

Only one independent source is present in the circuit

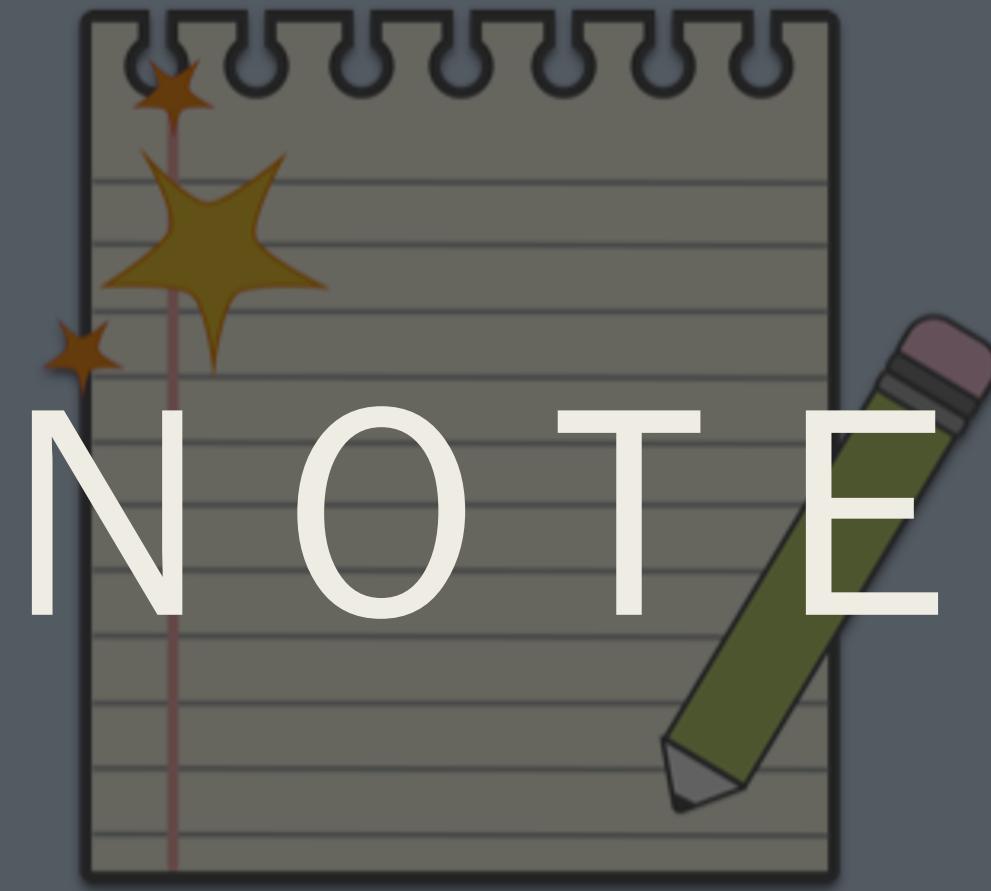No dependent source is present in the circuit




- The reciprocity theorem is applicable for both AC and DC circuits.

- The reciprocity theorem is applicable for both AC and DC circuits.
- While applying Reciprocity theorem, the circuit does not have time varying element.

- The reciprocity theorem is applicable for both AC and DC circuits.
- While applying Reciprocity theorem, the circuit does not have time varying element.
- **Using Reciprocity theorem, it is possible to conclude if a network is linear or non-linear.**

WHY ANOTHER THEOREM?

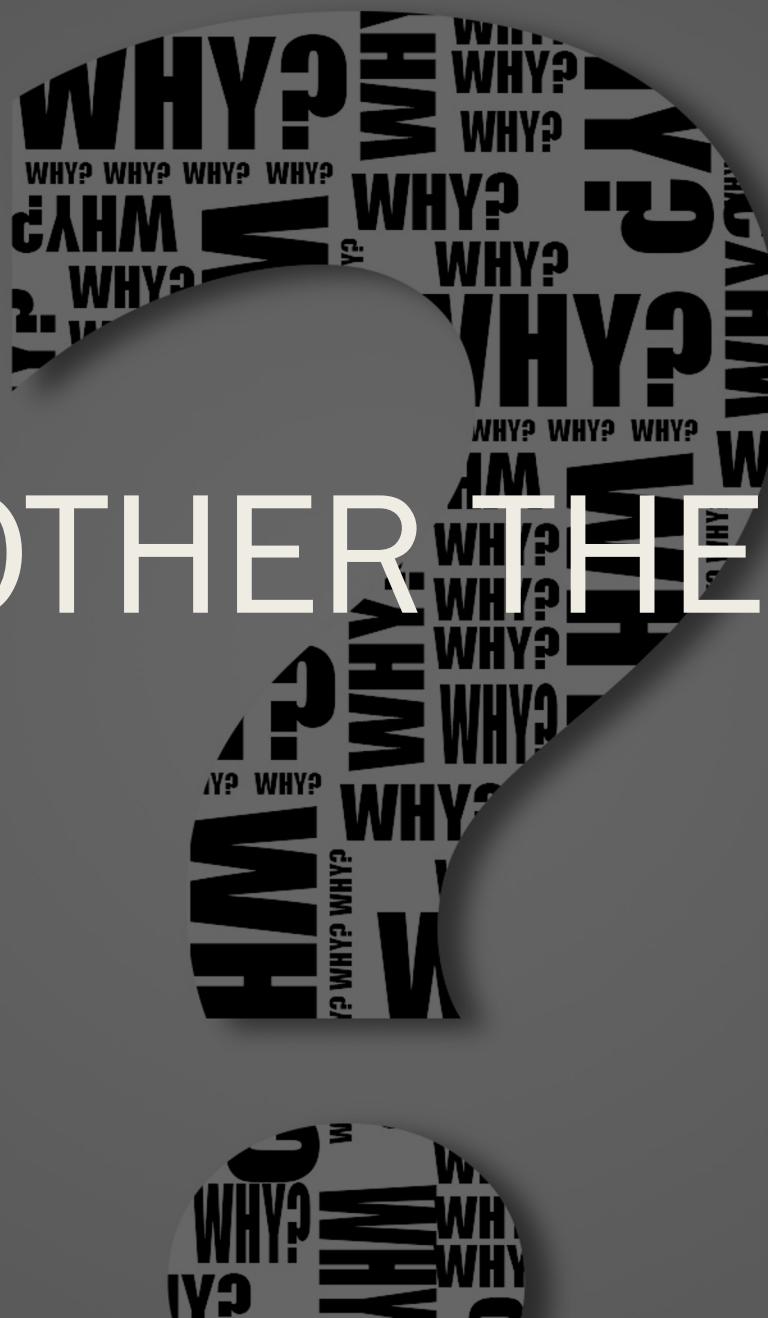

APPLICATIONS

- This theorem is applied to analyze ultrasound generated by high-intensity surface heating of elastic bodies.

- This theorem is applied to analyze ultrasound generated by high-intensity surface heating of elastic bodies.
- **Making many results GREATLY simpler, like topics in antennae, electromagnetism.**

- This theorem is applied to analyze ultrasound generated by high-intensity surface heating of elastic bodies.
- Making many results greatly simpler, like topics in antennae, electromagnetism.
- **Making impedance calculations**

- This theorem is applied to analyze ultrasound generated by high-intensity surface heating of elastic bodies.
- Making many results greatly simpler, like topics in antennae, electromagnetism.
- Making impedance calculations
- **Treating properties like Polarizations, magnetization like properties.**



KASHIF ZUHAIR

LIMITATIONS



WARNING

- Not applicable to the circuits consisting of any time varying element.

- Not applicable to the circuits consisting of any time varying element.
- Not applicable to the circuits consisting of the dependent source even it is linear.

- Not applicable to the circuits consisting of any time varying element.
- Not applicable to the circuits consisting of the dependent source even it is linear.
- **Not applicable to the circuits consisting of non-linear elements like diode, transistor.**



EXAMPLE

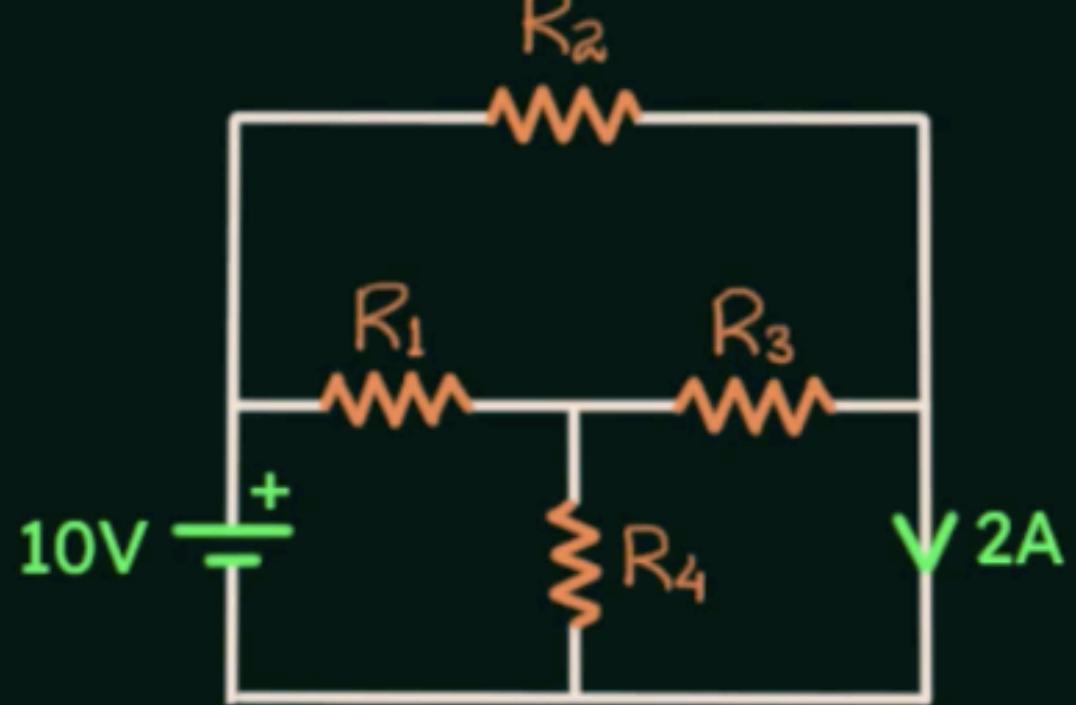


Fig.(a)

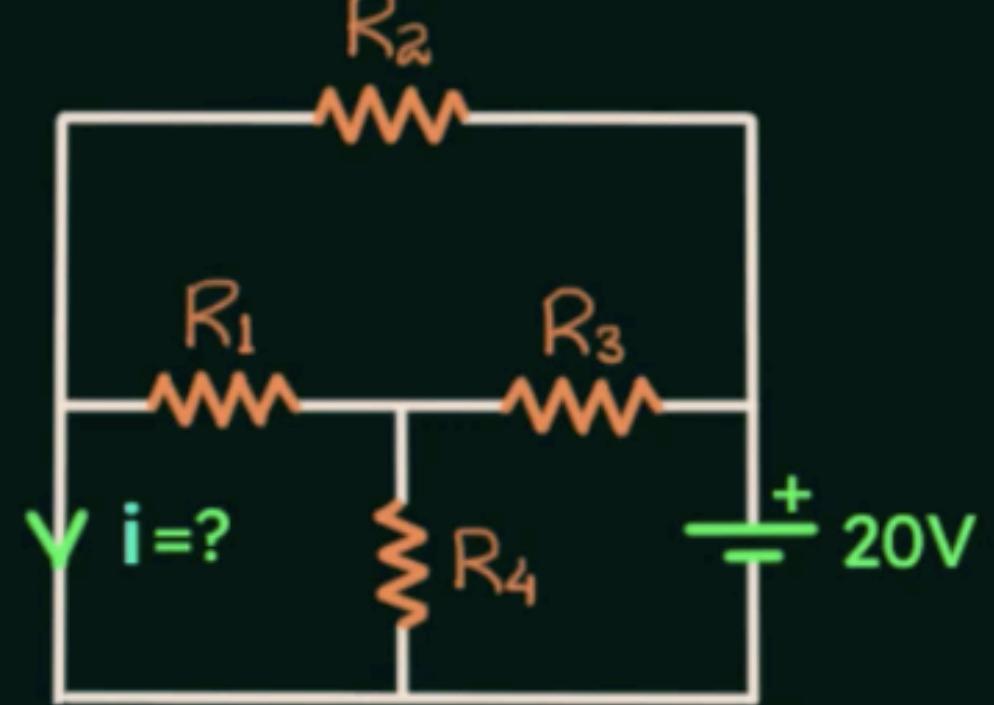


Fig.(b)

USING DATA GIVEN IN FIGURE (A), FIND THE VALUE OF CURRENT IN FIGURE (B).

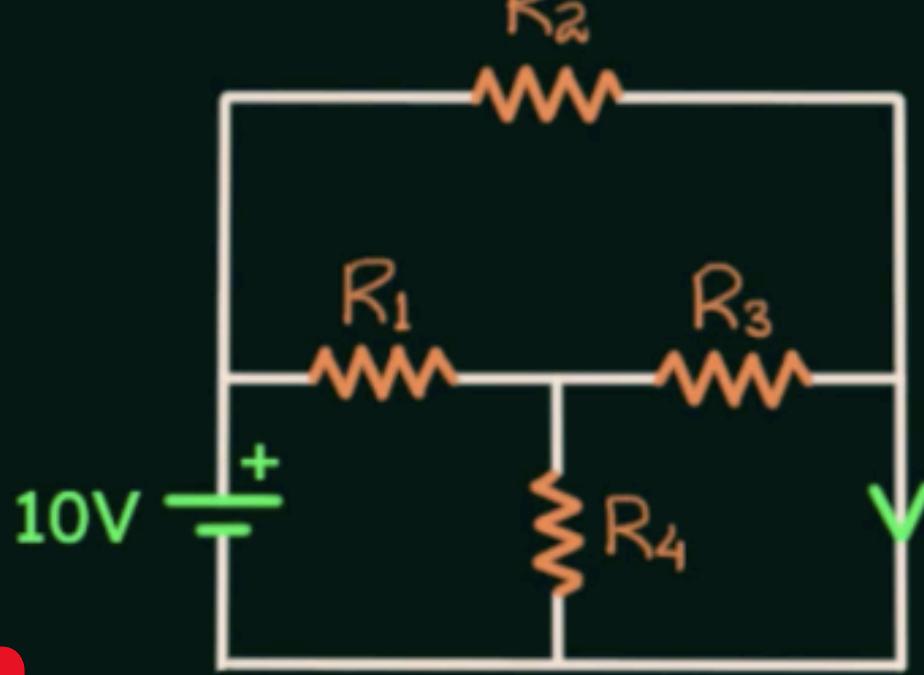


Fig.(a)

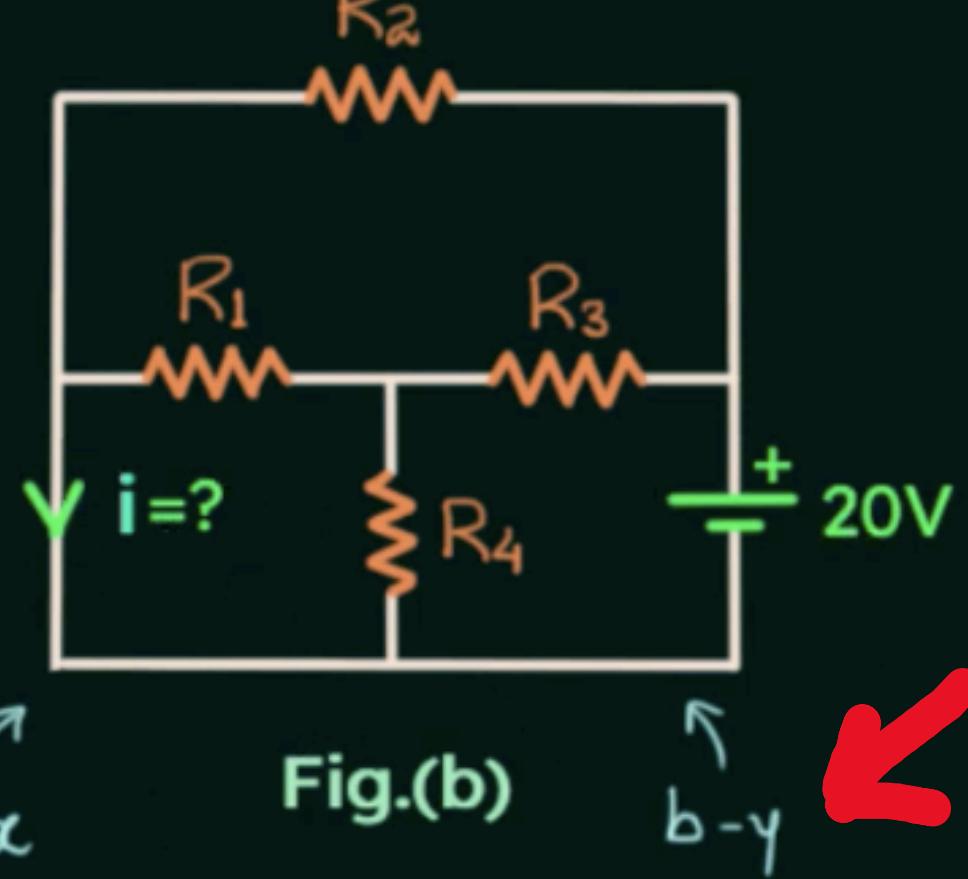


Fig.(b)

LET'S NAME THE BRANCHES FIRST.



LET'S
ANALYZE

■ All linear elements ?

- Res / exc = mho (or) ohm ?
- One independent source ?
- No dependent source ?

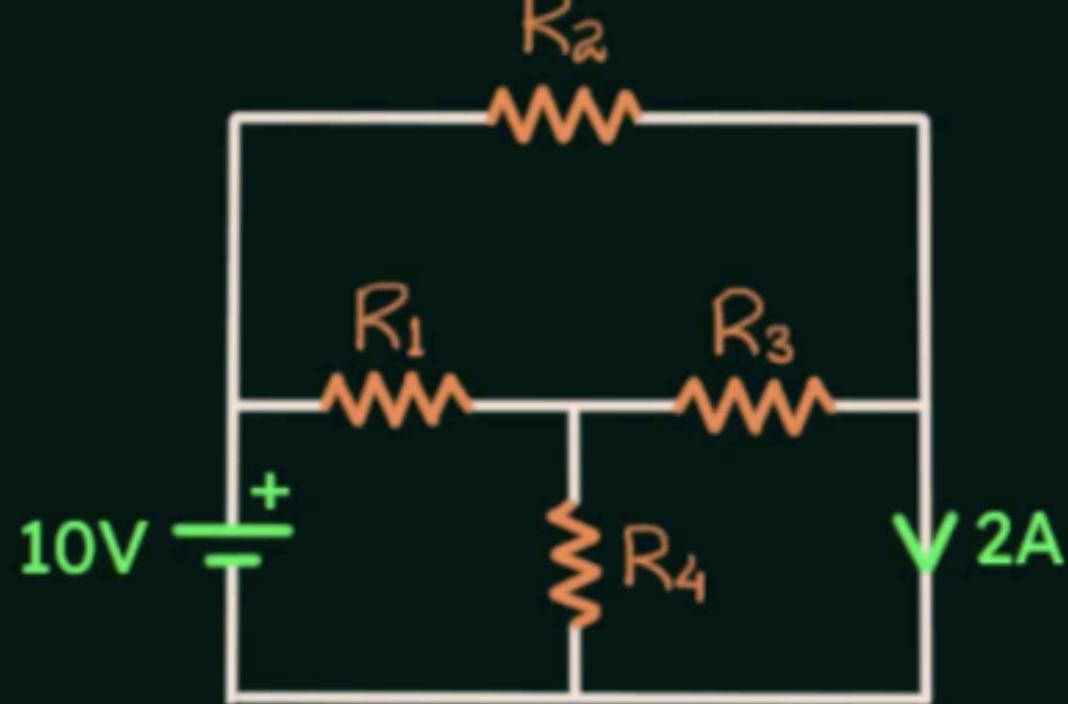


Fig.(a)

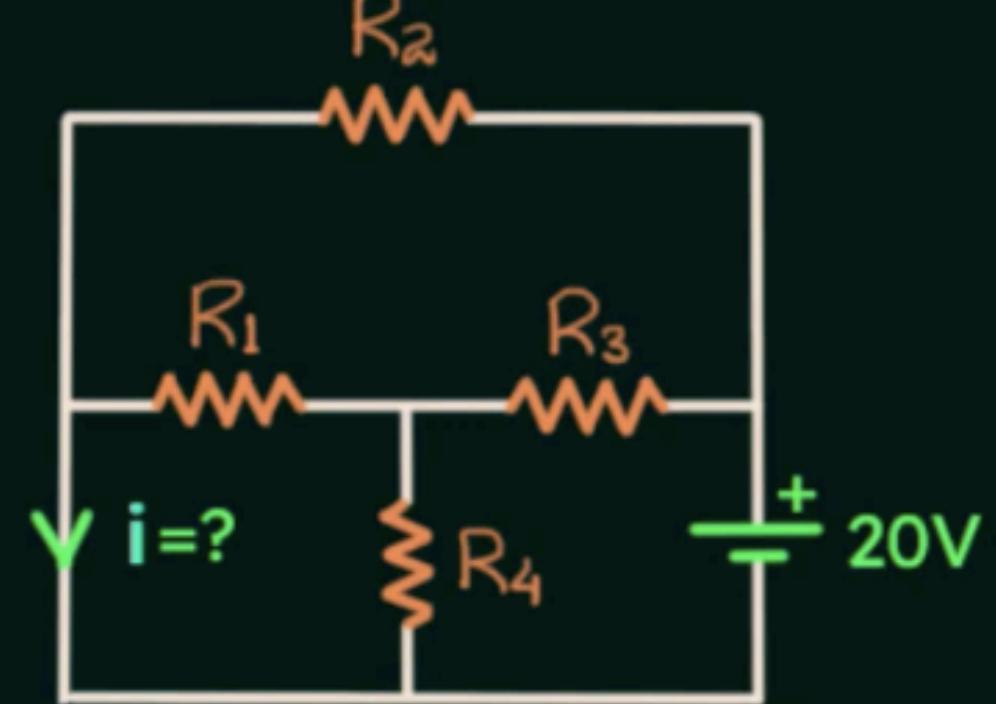


Fig.(b)

USING DATA GIVEN IN FIGURE (A), FIND THE VALUE OF CURRENT IN FIGURE (B).

■ All linear elements

- Res / exc = mho (or) ohm ?
- One independent source ?
- No dependent source ?



- All linear elements



■ Res / exc = mho (or) ohm ?

- One independent source ?
- No dependent source ?

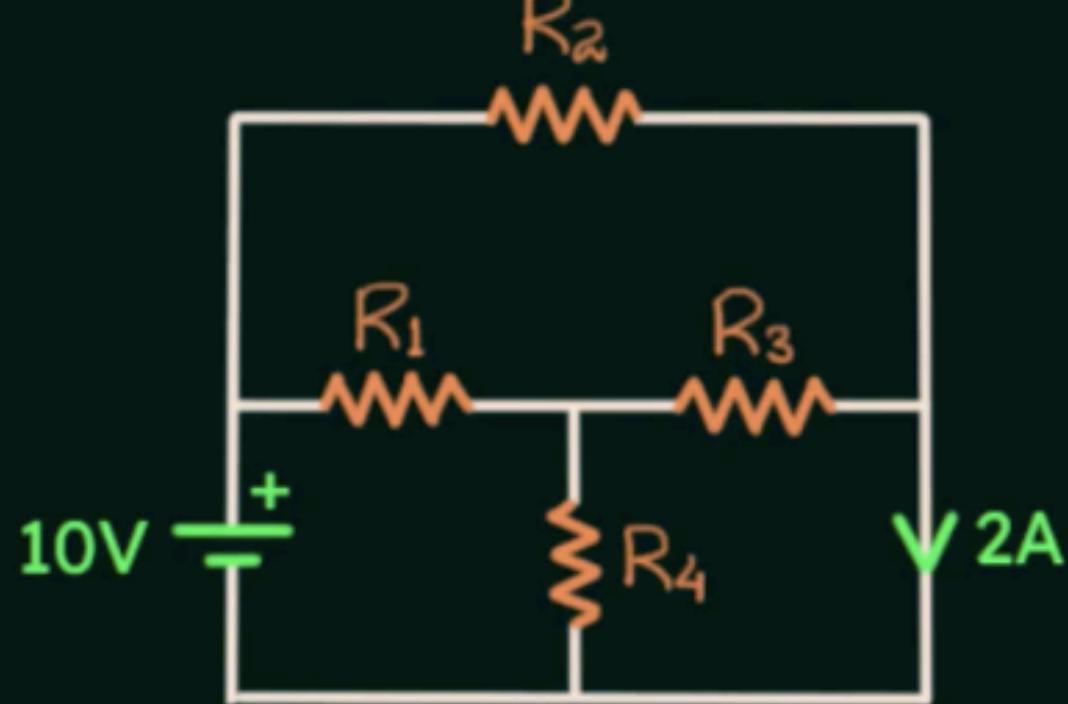


Fig.(a)

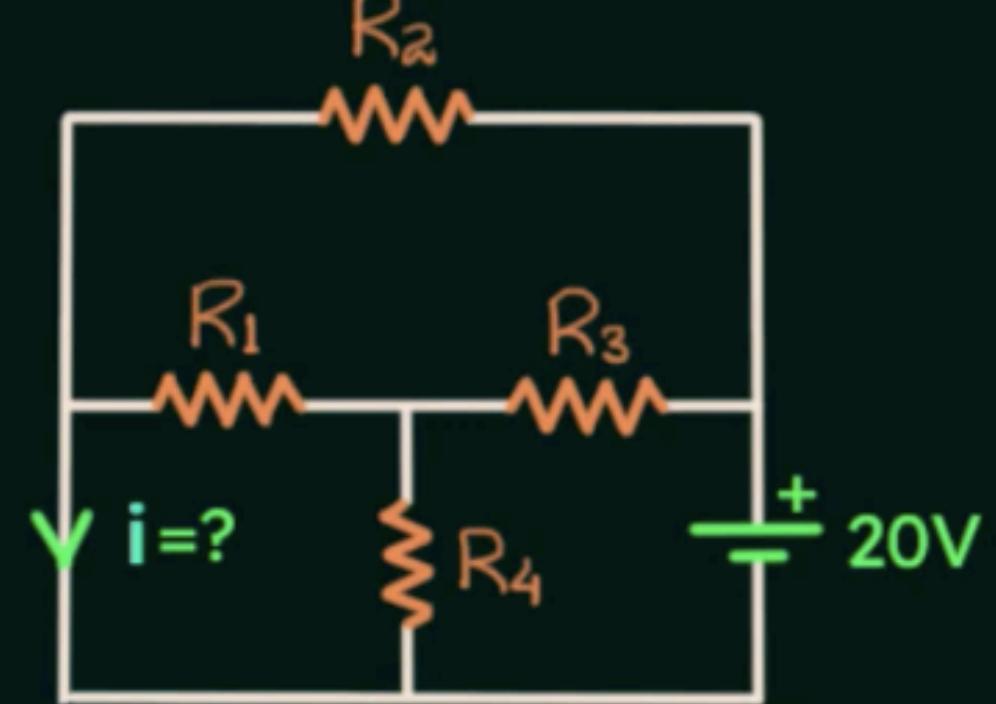


Fig.(b)

USING DATA GIVEN IN FIGURE (A), FIND THE VALUE OF CURRENT IN FIGURE (B).

- All linear elements



■ Res / exc = mho (or) ohm



- One independent source ?
- No dependent source ?

- All linear elements ? 
- Res / exc = mho (or) ohm ? 

■ One independent source ?

- No dependent source ?

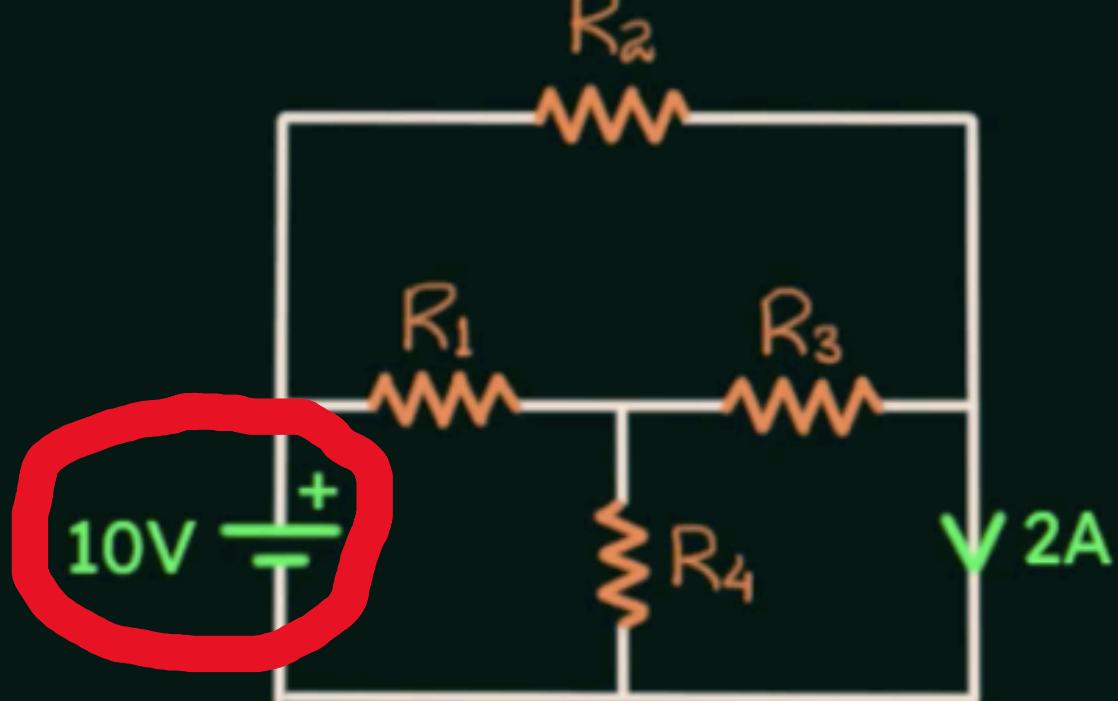


Fig.(a)

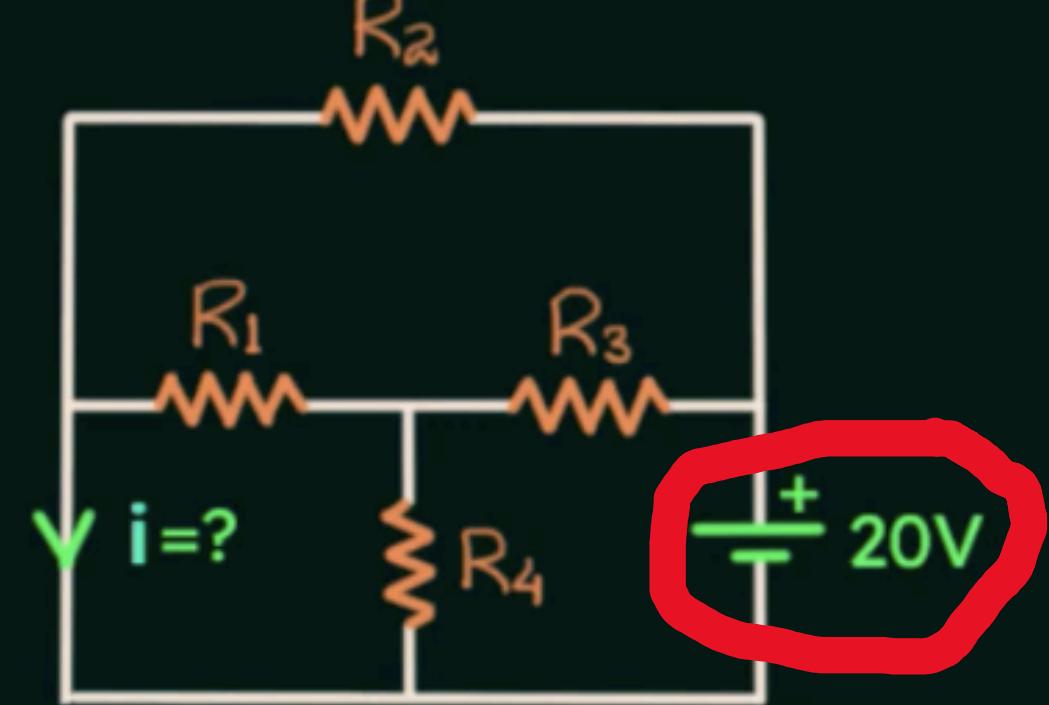


Fig.(b)

USING DATA GIVEN IN FIGURE (A), FIND THE VALUE OF CURRENT IN FIGURE (B).

- All linear elements ?



- Res / exc = mho (or) ohm ?



■ One independent source ?



- No dependent source ?

- All linear elements ? 
- Res / exc = mho (or) ohm ? 
- One independent source ? 

■ No dependent source ?

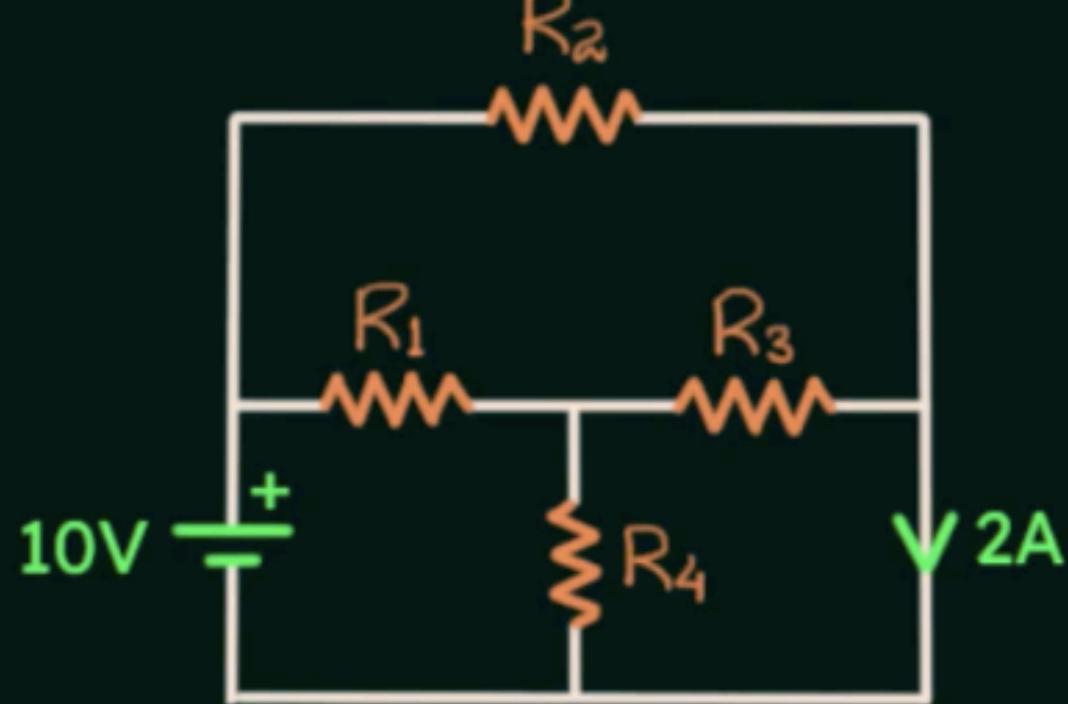


Fig.(a)

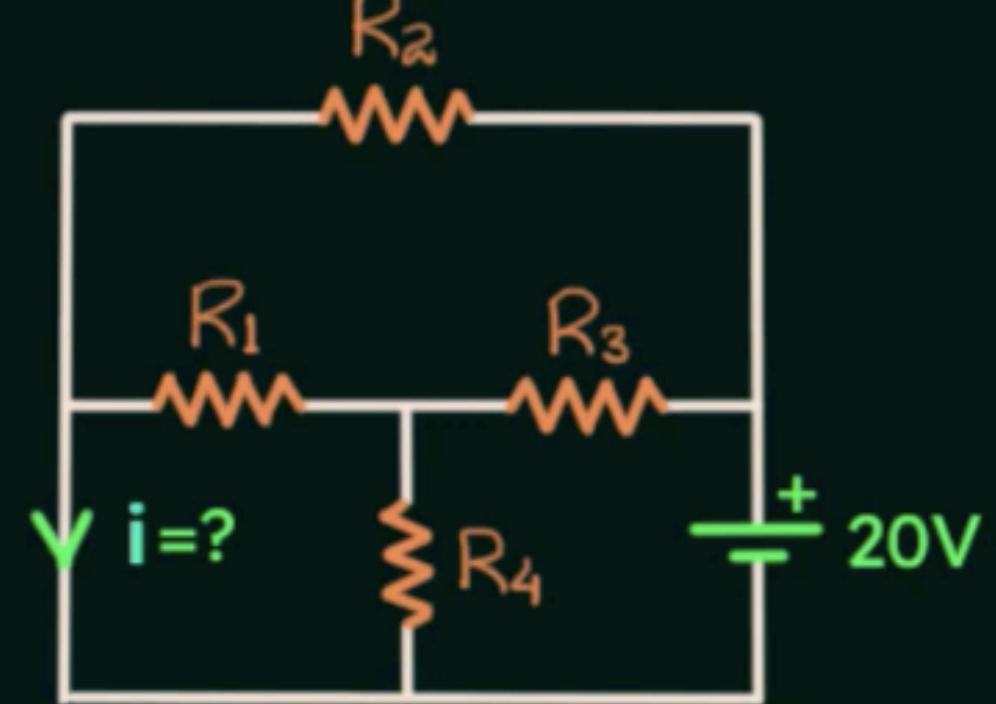



Fig.(b)

USING DATA GIVEN IN FIGURE (A), FIND THE VALUE OF CURRENT IN FIGURE (B).


- All linear elements ? 
- Res / exc = mho (or) ohm ? 
- One independent source ? 

■ No dependent source ?




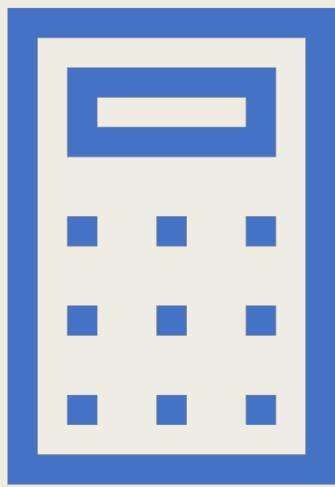


CALCULATIONS

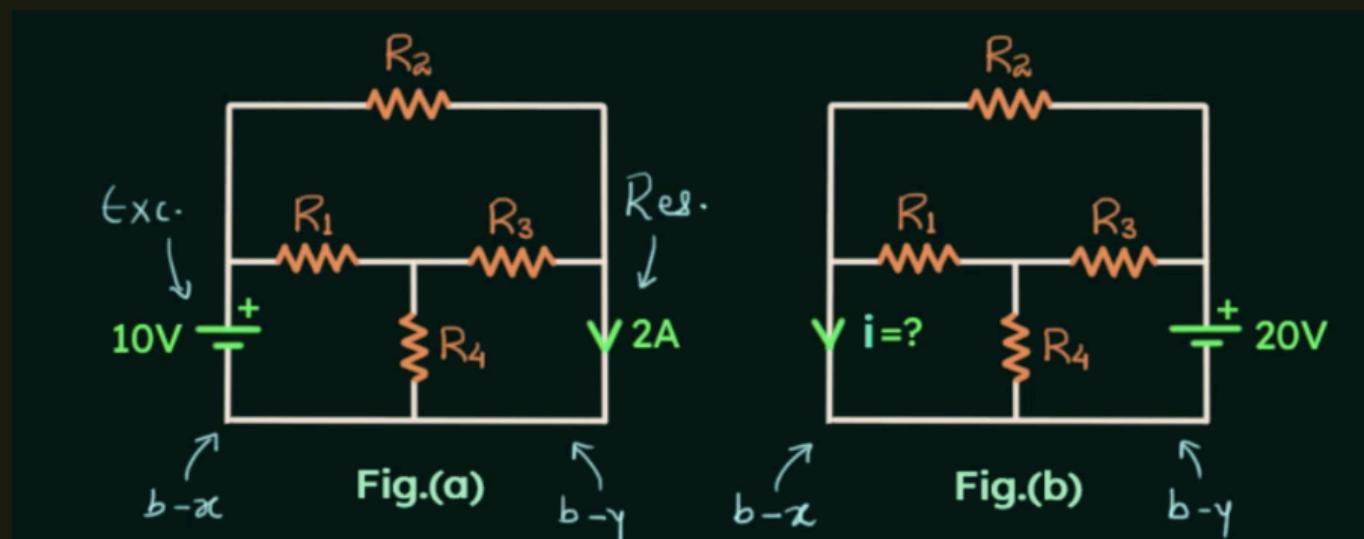

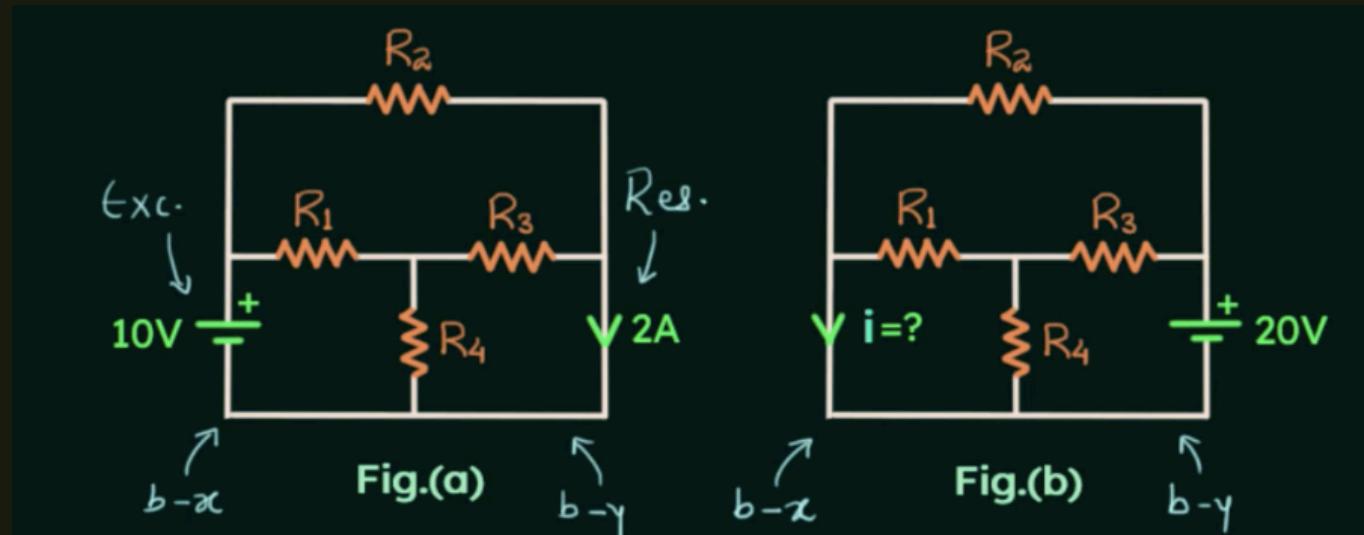
- Ratio of Res and excit. in left side = $2 / 10$
- Ratio of Res and excit. In right side = $i / 20$
- FROM RECIPROCITY THEOREM
- $2 / 10 = i / 20$
- $i = 4 \text{ Amp.}$
[our answer]



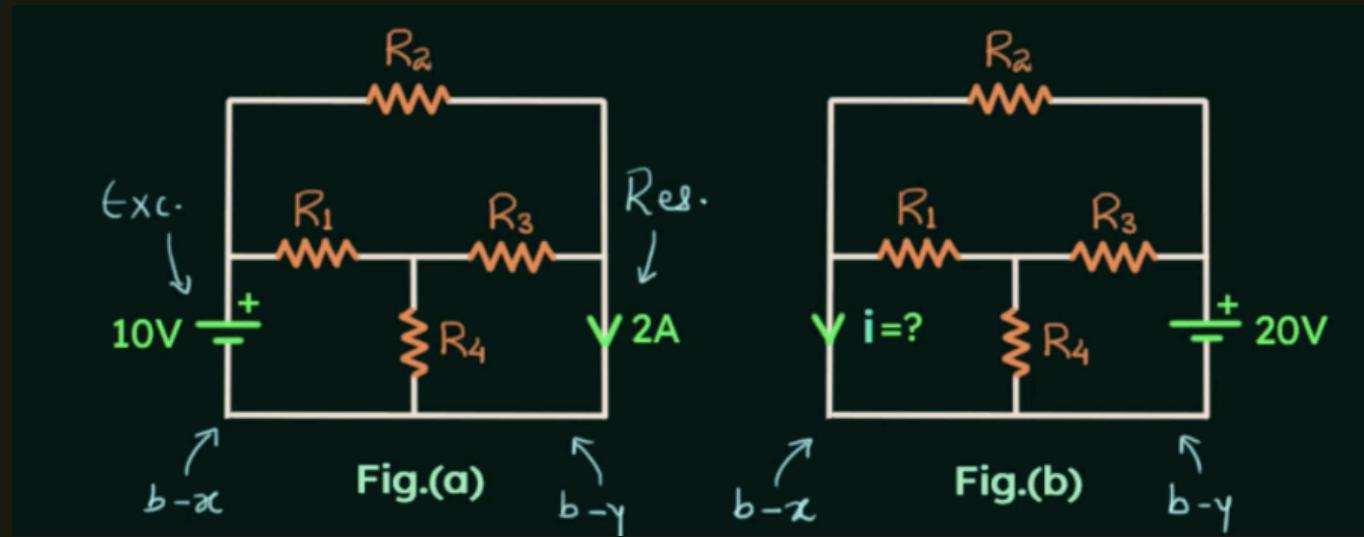
- Ratio of Res and excit. In left side = $2 / 10$
- Ratio of Res and excit. In right side = $i / 20$
- FROM RECIPROCITY THEOREM
- $2 / 10 = i / 20$
- $i = 4 \text{ Amp.}$
[our answer]



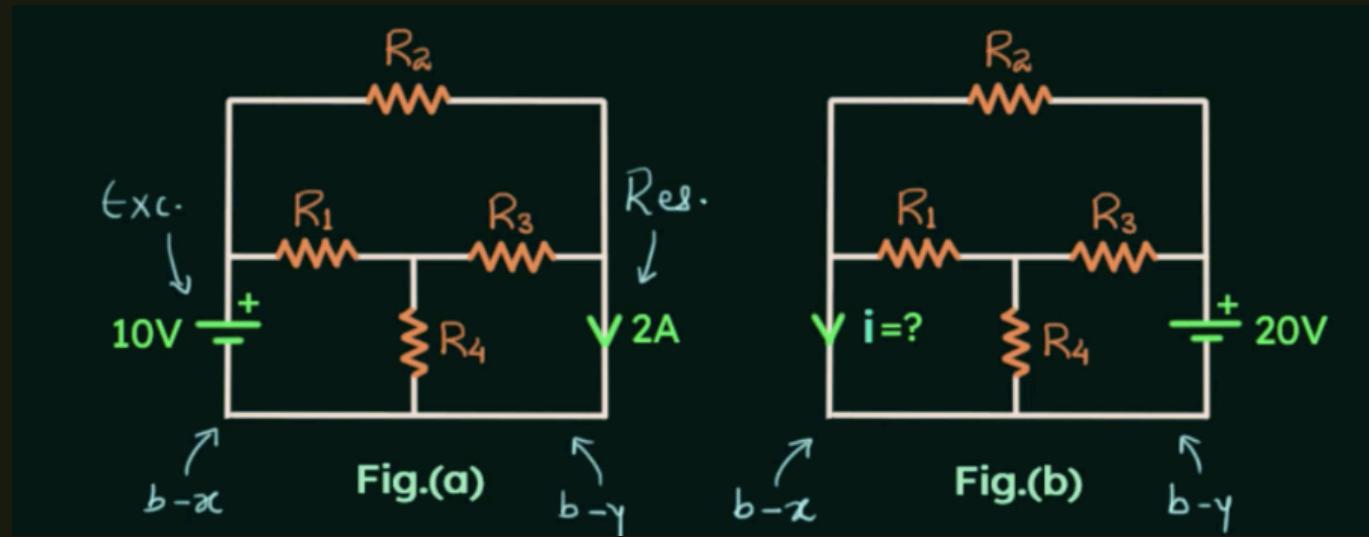- Ratio of Res and excit. In left side = $2 / 10$
- Ratio of Res and excit. In right side = $i / 20$
- **FROM RECIPROCITY THEOREM**
- $2 / 10 = i / 20$
- $i = 4 \text{ Amp.}$
[our answer]



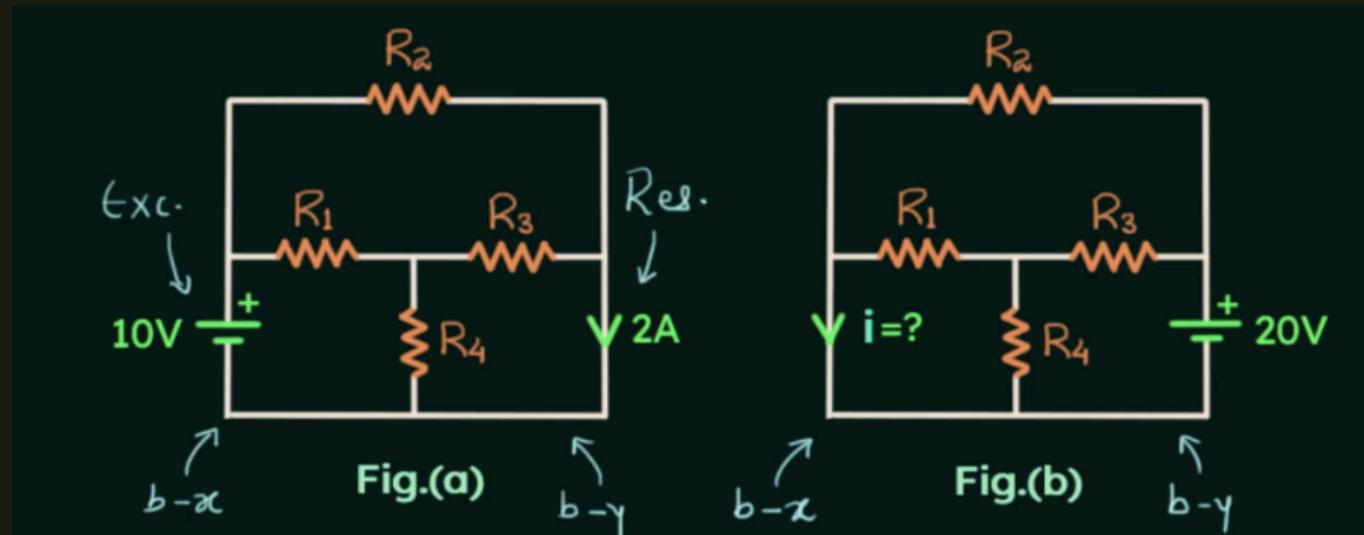
- Ratio of Res and excit. In left side = $2 / 10$
- Ratio of Res and excit. In right side = $i / 20$
- FROM RECIPROCITY THEOREM
- $2 / 10 = i / 20$
- $i = 4$ Amp.
[our answer]



- Ratio of Res and excit. In left side = $2 / 10$
- Ratio of Res and excit. In right side = $i / 20$
- FROM RECIPROCITY THEOREM
- $2 / 10 = i / 20$

■ $i = 4 \text{ Amp.}$

[our answer]

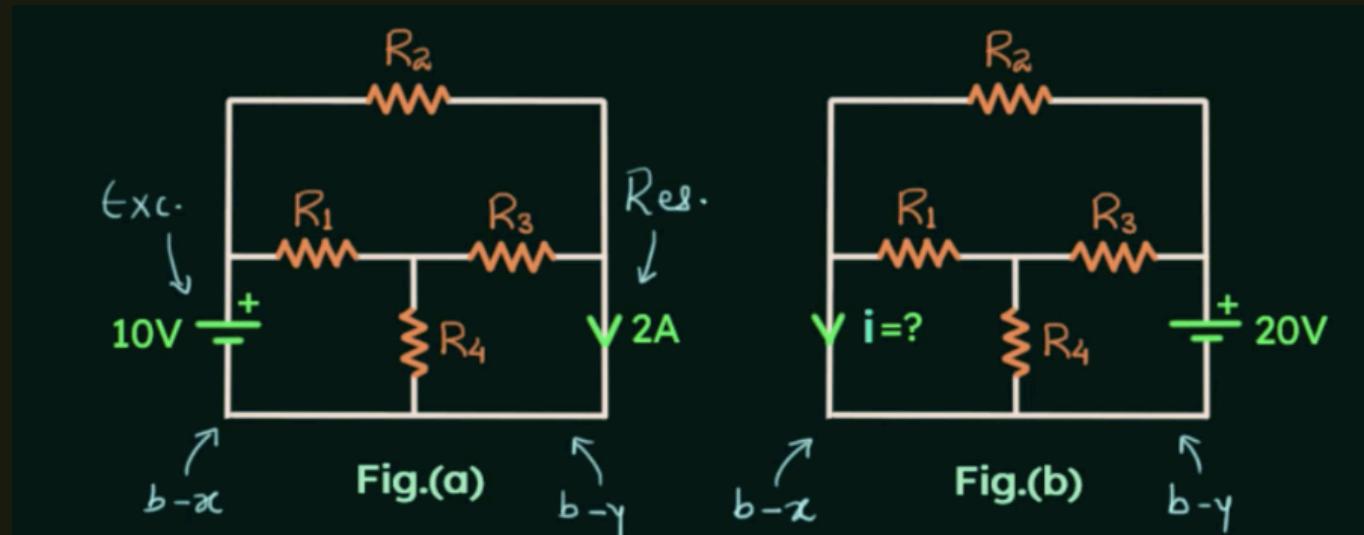

- Ratio of Res and excit. In left side = $2 / 10$
- Ratio of Res and excit. In right side = $i / 20$
- FROM RECIPROCITY THEOREM
- $2 / 10 = i / 20$

$i = 4 \text{ Amp.}$
[our answer]

SOURCES





- Neso academy (YouTube)
- Electrical4u
- Electrical voice
- Wikipedia

THANK You
FOR Your
TIME



ALL NEEDS
MEET
MEET
3D AM
REVIEW
OR